

Computer Assignment 1

RISC-V Processor

Single Cycle Approach

November 23rd, 2024



Bardia Amirian | 810101605
Amirreza Nadi Chaghadari | 810101538

Digital Systems 2

Dr. Safari

Table of Contents

Problem Description	1
Instruction Formats	2
R-Type Instructions	2
Instruction format	2
Instruction Execution Table.....	2
I-Type Instructions	3
Instruction format	3
Instruction Execution Table.....	3
S-Type Instructions.....	4
Instruction format	4
Instruction Execution Table.....	4
J-Type Instructions	5
Instruction format	5
Instruction Execution Table.....	5
B-Type Instructions	6
Instruction format	6
Instruction Execution Table.....	6
U-Type Instructions	7
Instruction format	7
Instruction Execution Table.....	7
Datapath Design.....	8
Abstract Block Diagram	8
Designing Components.....	10
MUX	10
Adder	11
ALU	12
Immediate Extension	15

Table of Contents

PC (Program counter)	16
Instruction Memory	17
Data Memory	18
Register File.....	19
Assembling Datapath.....	20
Controller	21
Top Module	22
Testing Phase	23
Writing Assembly Code	23
Generating RISC-V Machine Code.....	25
Testbench and Results	27

Table of Figures

Figure 1. Datapath Block Diagram.....	8
Figure 2. MUX Verilog Description	10
Figure 3. MUX Testbench Results	10
Figure 4. Adder Verilog Description.....	11
Figure 5. Adder Testbench Results.....	11
Figure 6. ALU Verilog Description.....	12
Figure 7. ALU Testbench	13
Figure 8. ALU Testbench Results	14
Figure 9. Immediate Extension Verilog	15
Figure 10. Program Counter Verilog Description	16
Figure 11. Instruction Memory Verilog Description.....	17
Figure 12. Data Memory Verilog	18
Figure 13. Register File	19
Figure 14. Datapath Module Verilog Description.....	20
Figure 15. Controller: Result Source Handling Always Block.....	21
Figure 16. Top Module Verilog Description	22
Figure 17. Minimum Finder Code in C language	23
Figure 18. Assembly-Friendly Minimum Finder Code.....	23
Figure 19. Assembly Code for Minimum Finder	24
Figure 20. Assembly and Machine Code	25
The assembly codes are translated to RISC-V machine language in Hex (the related hex instruction of each line of the assembly code is shown in Figure 21)..	
Figure 22. Top Module Testbench	27
Figure 23. Testbench Results.....	27

Table of Tables

Table 1. T-Type Instruction Format	2
Table 2. R-Type Instruction Execution Table	2
Table 3. I-Type Instruction Format	3
Table 4. I-Type Instruction Execution Table	3
Table 5. S-Type Instruction Format	4
Table 6. S-Type Instruction Execution Table.....	4
Table 7. J-Type Instruction Format	5
Table 8. J-Type Instruction Execution Table	5
Table 9. B-Type Instruction Format	6
Table 10. B-Type Instruction Execution Table	6
Table 11. U-Type Instruction format.....	7
Table 12. U-Type Instruction Execution Table	7
Table 13. ALU Op-Code Table	12
Table 14. Immediate Formatting	15

Problem Description

We are to design a simplified version of the RISC-V processor, using single-cycle approach. It means that each instruction takes exactly one clock cycle to execute. Here are the list of instructions we are expected to implement:

R-Type¹: add, sub, and, or, slt

I-Type²: lw, addi, xori, ori, slti, jalr

S-Type³: sw

J-Type⁴: jal

B-Type⁵: beq, bne

U-Type⁶: lui

Each of these instructions have their own format, thus requiring the datapath to include appropriate paths for the data to flow accordingly.

Once we designed the processor, we are to test it by running a code on it which searches for the minimum of an array with 10 elements.

¹ Register Type

² Immediate Type

³ Store Type

⁴ Jump Type

⁵ Branch Type

⁶ Upper Type

Instruction Formats

R-Type Instructions

Instruction format

Luckily, all R-Type instructions we are to implement are well-defined and are almost the same. The only thing that differs between them is what the ALU⁷ does with its inputs. the overall form of these instructions looks like this:

Table 1. T-Type Instruction Format

31	25	24	20	19	15	14	12	11	7	6	0
f ₇		r _{s2}		r _{s1}		f ₃		r _d		OPC	

Instruction Execution Table

Table 2. R-Type Instruction Execution Table

add	$r_d = r_{s1} + r_{s2}$
sub	$r_d = r_{s1} - r_{s2}$
and	$r_d = r_{s1} \& r_{s2}$ (bitwise)
or	$r_d = r_{s1} r_{s2}$ (bitwise)
slt	$r_d = r_{s1} < r_{s2} ? 1 : 0$

⁷ Arithmetic-Logic Unit (ALU): The part that handles arithmetic and logical calculations.

I-Type Instructions

Instruction format

Immediate type instructions of this computer assignments have 3 types:

1. The arithmetic type which includes addi, ori, xori, and slti
2. Loading type which includes lw
3. Jumping type which includes jalr

Table 3. I-Type Instruction Format

31	20	19	15	14	12	11	7	6	0
Imm ⁸ [11:0]				r _{s1}	f ₃	r _d		OPC	

Instruction Execution Table

Table 4. I-Type Instruction Execution Table

addi	$r_d = r_{s1} + Imm$ (Sign-Extended)
ori	$r_d = r_{s1} Imm$ (Sign-Extended)
xori	$r_d = r_{s1} \oplus Imm$ (Sign-Extended)
slti	$r_d = r_{s1} < Imm ? 1 : 0$ (Sign-Extended)
lw	$r_d = Mem^9[r_{s1} + Imm]$ (Signed-Extended)
jalr	$r_d = pc + 4$
	$pc = r_s + Imm$ (Signed-Extended)

⁸ Immediate

⁹ Memory

S-Type Instructions

Instruction format

This assignment includes only one S-Type instruction, sw.

Table 5. S-Type Instruction Format

31	25	24	20	19	15	14	12	11	7	6	0
Imm[11:5]		r _{s2}		r _{s1}		f ₃		Imm[4:0]		OPC	

Instruction Execution Table

Table 6. S-Type Instruction Execution Table

sw	$Mem[r_{s1} + Imm] = r_{s2}$ (Sign-Extended)
----	--

J-Type Instructions

Instruction format

This assignment includes only one J-Type instruction: jal

Table 7. J-Type Instruction Format

31	25	24	20	19	15	14	12	11	7	6	0
Imm[20, 10:1, 11, 19:12]								r_d	OPC		

The first thing to be noticed here, is how the immediate part contains bits 20:1, and not 19:0. This is because the value must be an integer coefficient of 4, meaning that its least significant 2 bits must be 0. Due to the weird choice made by the developers of RISC-V processor, the first one is ignored, but the second one must be included to avoid address exception! Therefore, the immediate could be interpreted like this:

$$Imm = \{Offset[20:2], 1'b0\}$$

There is also the weird format of giving the immediate, but it was another one of RISC-V processor's developers' choices we need to follow.

There is one more thing to be discussed here. If we do not specify r_d , the default value will be ra. But, this is not the concern of this assignment, since we are not implementing an assembler.

Instruction Execution Table

Table 8. J-Type Instruction Execution Table

jal	$r_d = pc + 4$ $pc = pc + Imm$ (Signed-Extended)
-----	---

B-Type Instructions

Instruction format

There are 2 branch instructions we are expected to implement: bne and beq. They both have this structure

Table 9. B-Type Instruction Format

31	25	24	20	19	15	14	12	11	7	6	0
Imm[12, 10:5]	r _{s2}			r _{s1}		f ₃		Imm[4:1, 11]	OPC		

What is to be noticed here (again!), is the weird format of the immediate. It is not saved consecutively, and does not end with 0. It has a formula like this:

$$Imm = \{Offset[12:2], 1'b0\}$$

Instruction Execution Table

Table 10. B-Type Instruction Execution Table

beq	$pc = r_{s1} == r_{s2} ? pc + Imm : pc + 4$
bne	$pc = r_{s1} \sim = r_{s2} ? pc + Imm : pc + 4$

U-Type Instructions

Instruction format

This assignment includes only one U-Type instruction: lui

Table 11. U-Type Instruction format

31	25	24	20	19	15	14	12	11	7	6	0
Imm[19:0]								r_d	OPC		

Instruction Execution Table

Table 12. U-Type Instruction Execution Table

lui	$r_d = \{Imm, 12'H000\}$ (Signed-Extended)
-----	--


With these tables at hand, we can design the datapath.

Datapath Design

Abstract Block Diagram

The block diagram of the datapath looks like this:

Figure 1. Datapath Block Diagram

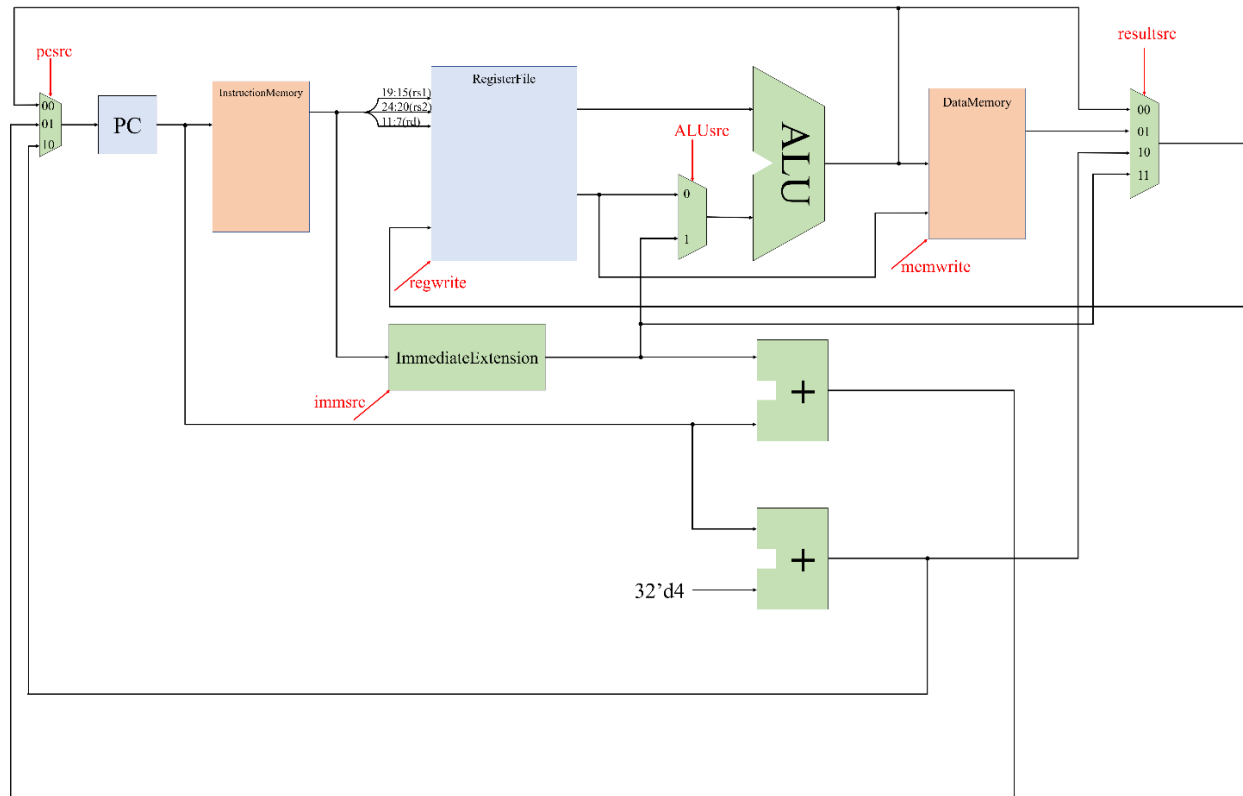

Where red signals come from the controller, edged connections (ones that are marked by a dot) mean the entire wire array is given to both branches, and rounded branches (at the input of the Register File) mean that the wire array is split into parts.

Here, the combination of “PC” and “Instruction Memory” handles the flow of the code being executed on the process. Instruction Memory’s output is connected to the “Register File” to address the source and destination registers. It is also given to the Immediate Extension block in order to extract immediate values out of it. The ALU has 2 inputs. One comes from the Register File itself, and the other is the output if a MUX choosing between another register or the immediate value. This allows the execution of R-Type and I-Type instructions. By connecting Register File’s second output to the input of “Data Memory”, the datapath becomes capable of executing “sw” instruction. Also, the output of the memory id connected to the input of the Register File, making “lw” instruction’s execution possible. Considering the fact that

the ALU has a “ZERO” flag, B-Type instructions are easily handled by subtracting the operands and using the ZERO flag to set PC’s next value. Also, J-Type instructions are easily done because of the two extra adders. As for the “lui” instruction, we can direct Immediate Extension’s output to the Register File’s input. Therefore, all of the given instructions can be executed using this datapath.

Next step is to design and implement each component used in the datapath, instantiate them, and assemble the datapath by wiring the instances together.

Designing Components

MUX¹⁰


Multiplexer is one of the easiest purely-combinational components we are to implement. The Verilog description of it looks like this:

Figure 2. MUX Verilog Description

```
1  `timescale 1ns/1ps
2
3  module MUX_TB();
4
5      parameter WL = 32, SIZE = 4;
6      parameter SELECT_SIZE = $clog2(SIZE);
7
8      reg [SIZE-1:0][WL-1:0] dataIN;
9      reg [SELECT_SIZE-1:0] select;
10
11      wire [WL-1:0] dataOUT;
12
13      MUX #(SIZE, WL) UUT (dataIN, select, dataOUT);
14
15      always #30 dataIN = {$random, $random, $random, $random, $random};
16
17      always #13 select = $random;
18
19      initial begin
20          #500 $stop;
21      end
22
23  endmodule
```

We also designed a simple testbench to test this MUX with random data, and got these results:

Figure 3. MUX Testbench Results

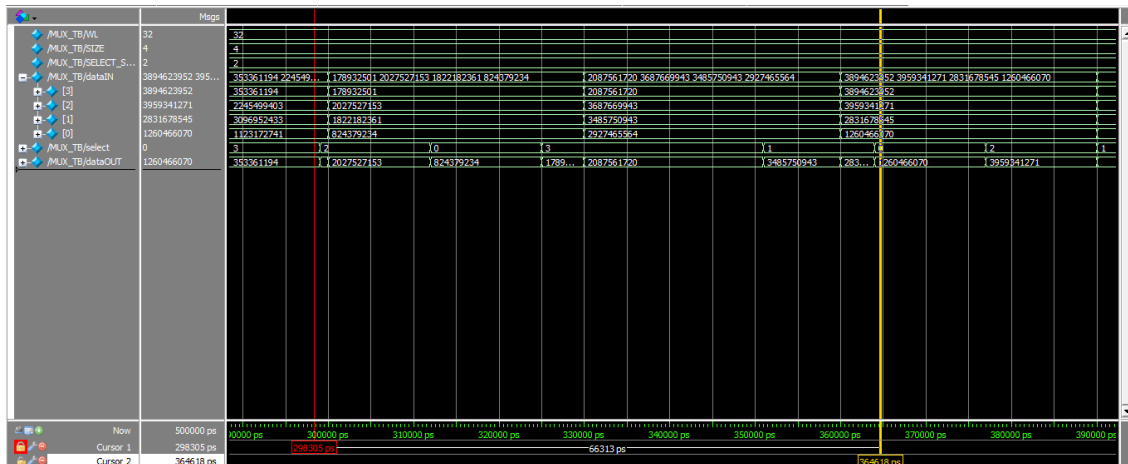

This waveform (the part between the two cursors) represents different things that could happen to the inputs, and the MUX's response to them, verifying the functionality of the MUX.

¹⁰ Multiplexer

Adder


Adder is also simple to implement. Here's the Verilog description:

Figure 4. Adder Verilog Description

```
15 module Adder #(parameter SIZE = 32) (A, B, S);  
16  
17     input [SIZE-1:0] A;  
18     input [SIZE-1:0] B;  
19     output [SIZE-1:0] S;  
20  
21     assign S = A + B;  
22 endmodule
```

As for the testing, this waveform confirms its functionality:

Figure 5. Adder Testbench Results

 

ALU

ALU can be simply implemented using an always block. But, we need to have a clear operation table first. Here's the one we used:

Table 13. ALU Op-Code Table

Op-Code ¹¹	Operation
000	Add
001	Subtract
010	AND
011	OR
100	SLT
101	XOR

Now we can describe it in Verilog. Here's the description:

Figure 6. ALU Verilog Description

```
26 module ALU #(parameter WL = 32) (OpCode, operand1, operand2, result, ZERO);
27
28     parameter    ADD = 3'b000,
29                 SUB = 3'b001,
30                 AND = 3'b010,
31                 OR  = 3'b011,
32                 SLT = 3'b100,
33                 XOR = 3'b101;
34
35     input [2:0] OpCode;
36     input signed [WL-1:0] operand1, operand2;
37     output signed [WL-1:0] result;
38     output ZERO;
39
40     reg signed [WL-1:0] result_temp;
41     assign result = result_temp;
42
43     always @(OpCode, operand1, operand2) begin
44         result_temp = {(WL){1'b0}};
45         case(OpCode)
46             ADD: begin result_temp = operand1 + operand2; end
47             SUB: begin result_temp = operand1 - operand2; end
48             AND: begin result_temp = operand1 & operand2; end
49             OR:  begin result_temp = operand1 | operand2; end
50             SLT: begin result_temp = (operand1 < operand2) ? {(WL-1){1'b0}}, 1'b1 : {(WL){1'b0}}; end
51             XOR: begin result_temp = operand1 ^ operand2; end
52             default: result_temp = operand1;
53         endcase
54     end
55
56     assign ZERO = &{result};
57 endmodule
```

¹¹ Operation Code

The inputs and output are defined as signed values, so that “slt” operation becomes possible. As for functionality confirmation, we used this testbench to test its response to different op-codes:

Figure 7. ALU Testbench


```

41  module ALU_TB();
42
43      parameter WL = 32;
44
45      parameter  ADD = 3'b000,
46                SUB = 3'b001,
47                AND = 3'b010,
48                OR  = 3'b011,
49                SLT = 3'b100,
50                XOR = 3'b101;
51
52      reg [2:0] OpCode;
53      reg signed [WL-1:0] operand1, operand2;
54      wire signed [WL-1:0] result;
55      wire ZERO;
56      ALU #(WL) UUT (OpCode, operand1, operand2, result, ZERO);
57
58      always #20 {operand1, operand2} = {$random, $random};
59
60      integer i;
61      initial begin
62          OpCode = ADD;
63          {operand1, operand2} = {$random, $random};
64          for (i = ADD ; i <= XOR ; i = i + 1) begin
65              OpCode = i;
66              #100;
67          end
68          #1
69          operand1 = 32'd25;
70          operand2 = -32'd25;
71          OpCode = ADD;
72          #20 $stop;
73      end
74
75  endmodule

```

The results are shown in the next page.

Figure 8. ALU Testbench Results

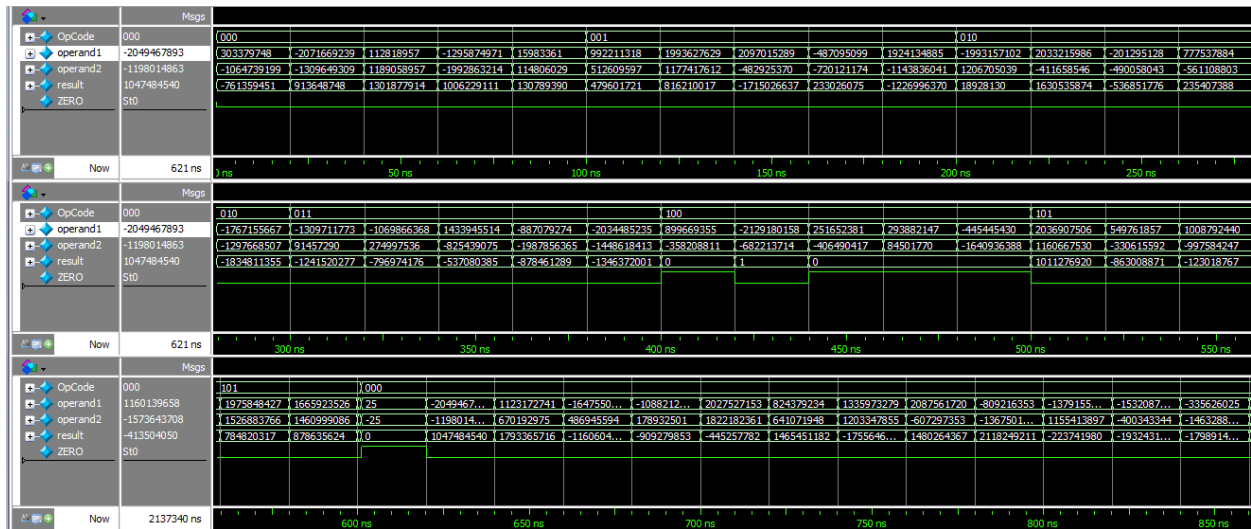

Immediate Extension

This part is nothing but wiring and multiplexing, and is done due to this table:

Table 14. Immediate Formatting

immsrc	Type	Size	Format
000	I-Type	12	{{20{Instr[31]}}, Instr[31:20]}
001	S-Type	12	{{20{Instr[31]}}, Instr[31:25], Instr[11:7]}
010	B-Type	13	{{20{Instr[31]}}, Instr[7], Instr[30:25], Instr[11:8], 1'b0}
011	J-Type	21	{{12{Instr[31]}}, Instr[19:12], Instr[20], Instr[30:21], 1'b0}
100	U-Type	21	{Instr[31:12], 12'b0}

Where “Instr” stands for instruction. The rest is just a matter of writing this in Verilog.

Figure 9. Immediate Extension Verilog

```

59 module ImmediateExtension (ImmSrc, Inst, Imm);
60
61     parameter [2:0] I_TYPE = 2'b000,
62                     S_TYPE = 2'b001,
63                     B_TYPE = 2'b010,
64                     J_TYPE = 2'b011,
65                     U_Type = 2'b100;
66
67     input  [2:0] ImmSrc;
68     input  [31:0] Inst;
69     output [31:0] Imm;
70
71     reg [31:0] Imm_temp;
72     assign Imm = Imm_temp;
73
74     always @(ImmSrc, Inst) begin
75         Imm_temp = 32'b0;
76         case(ImmSrc)
77             I_TYPE: begin Imm_temp = {{20{Inst[31]}}, Inst[31:20]}; end
78             S_TYPE: begin Imm_temp = {{20{Inst[31]}}, Inst[31:25], Inst[11:7]}; end
79             B_TYPE: begin Imm_temp = {{20{Inst[31]}}, Inst[7], Inst[30:25], Inst[11:8], 1'b0}; end
80             J_TYPE: begin Imm_temp = {{12{Inst[31]}}, Inst[19:12], Inst[20], Inst[30:21], 1'b0}; end
81             U_Type: begin Imm_temp = {Inst[31:12], 12'b0}; end
82             default: Imm_temp = 32'b0;
83         endcase
84     end
85
86 endmodule

```

With this, all combinational components are ready. The rest of the components are sequential. But due to their simplicity¹², we did not use “Huffman Coding Style” to implement them.

¹² All of them are simple storage units, making them easy to describe in a single always block.

PC (Program counter)

PC is just a simple register. Here's how it's described in Verilog:

Figure 10. Program Counter Verilog Description

```
85
86  module ProgramCounter #(parameter SIZE = 32) (parallelIN, clk, rst, parallelOUT);
87
88      input [SIZE-1:0] parallelIN;
89      input clk, rst;
90      output [SIZE-1:0] parallelOUT;
91
92      reg [SIZE-1:0] Storage;
93      assign parallelOUT = Storage;
94
95      always @(posedge rst, posedge clk) begin
96          if(rst) Storage <= {(SIZE){1'b0}};
97          else    Storage <= parallelIN;
98      end
99
100  endmodule
```

The rest of the components are memory-type ones. For better test-automation, we decided to use some extra files to store some pre-determined data in them.

Instruction Memory

We decided to save the instructions inside a file and read the file upon simulation. Here's how it's done:

Figure 11. Instruction Memory Verilog Description

```
102
103     module InstructionMemory (pc, instruction);
104
105
106         input  [31:0] pc;
107         output [31:0] instruction;
108
109         reg [7:0] instMem [$pow(2, 16)-1:0];
110
111         wire [31:0] adr;
112         assign adr = {pc[31:2], 2'b00};
113
114         initial $readmemh("Ins_Fin.mem", instMem);
115
116         assign inst = {instMem[adr + 3], instMem[adr + 2], instMem[adr + 1], instMem[adr]};
117
118     endmodule
```

Thankfully, Verilog has the “\$readmemh” function and we do not need to read the file line-by-line manually. The file must have “.mem” postfix, and each line of it must contain 2 hexadecimal digits.

Data Memory

This memory needs to be loaded as well, but it also needs initialization to get the data we aim to sort. Therefore, we decided to do the initialization upon the negative edge of the restart signal. Here's how the Verilog description looks like:

Figure 12. Data Memory Verilog

```
121 module DataMemory (addressIN, dataIN, writeEN, clk,rst, dataOUT);
122
123     input [31:0] addressIN;
124     input [31:0] dataIN;
125     input clk,rst, writeEN;
126     output [31:0] dataOUT;
127
128
129     reg [7:0] dataMem [$pow(2, 16)-1:0];
130
131     wire [31:0] adr;
132     assign adr = {addressIN[31:2], 2'b00};
133
134     always @(negedge rst) begin
135         $readmemh("Data.mem", dataMem);
136     end
137
138     initial $readmemh("Data.mem", dataMem);
139
140     integer i;
141     always @(posedge clk, posedge rst) begin
142         if(rst) begin
143             for(i = 0 ; i < $pow(2, 16); i = i + 1) dataMem[i] = 0;
144         end
145         else begin
146             if (writeEN)
147                 {dataMem[adr + 3], dataMem[adr + 2], dataMem[adr + 1], dataMem[adr]} <= dataIN;
148             end
149         end
150
151
152     assign dataOUT = {dataMem[adr + 3], dataMem[adr + 2], dataMem[adr + 1], dataMem[adr]};
153
154 endmodule
```

Register File

This part is easy, since it is just a simple double-output single-input register array. Here's the Verilog code:

Figure 13. Register File

```
105 module RegisterFile (rs1, rs2, rd, writeData, regwrite, clk, rst, data1, data2);
106
107     input [4:0] rs1, rs2, rd;
108     input [31:0] writeData;
109     input regwrite;
110     input clk, rst;
111     output [31:0] data1, data2;
112
113     reg [31:0][31:0] RegFile;
114
115     always @(posedge clk, posedge rst) begin
116         if(rst) RegFile = 0;
117         else begin
118             if(regwrite & (rd != 5'b00000)) RegFile[rd] <= writeData;
119         end
120     end
121
122     assign data1 = RegFile[rs1];
123     assign data2 = RegFile[rs2];
124
125 endmodule
```

What is important here, is line 118. Writing in “ZERO” register is not allowed. It must always remain 0. The rest is just a matter of multiplexing.

With this, all the components are ready, allowing us to proceed to the next phase.

Assembling Datapath

With all the components ready at hand, we can assemble the datapath by instantiating the components and wiring them together. Here's how the Verilog code looks like:

Figure 14. Datapath Module Verilog Description

```
180 module Datapath(pcsrc, ImmSrc, regwrite, ALUSrc, OpCode, memwrite, resultsrc, clk,rst, ZERO, instruction);
181
182     input regwrite, ALUSrc, memwrite;
183     input [1:0] pcsrc, ImmSrc, resultsrc;
184     input [2:0] OpCode;
185     input clk,rst;
186     output ZERO;
187     output [31:0] instruction;
188
189     wire [31:0] PCIN, PCOUT;
190     ProgramCounter #(32) PC (.parallelIN(PCIN), .clk(clk),.rst(rst), .parallelOUT(PCOUT));
191
192     InstructionMemory IMEM (.pc(PCOUT), .instruction(instruction));
193
194     wire [31:0] data1, data2, writeData;
195     RegisterFile regfile (.rs1(instruction[19:15]), .rs2(instruction[24:20]), .rd(instruction[11:7]),
196     .writeData(writeData), .regwrite(regwrite), .clk(clk),.rst(rst), .data1(data1), .data2(data2));
197
198     wire [31:0] immediate, ALU_data2;
199     MUX #(2, 32) ALU_input_MUX (.dataIN({data2, immediate}), .select(ALUSrc), .dataOUT(ALU_data2));
200
201     wire [31:0] ALU_out;
202     ALU #(32) (.OpCode(OpCode), .operand1(data1), .operand2(ALU_data2), .result(ALU_out), .ZERO(ZERO));
203
204     wire [31:0] DataMemOut;
205     DataMemory DMEM (.addressIN(ALU_out), .dataIN(data2), .writeEN(memwrite), .clk(clk),.rst(rst), .dataOUT(DataMemOut));
206
207     ImmediateExtension imm_ext (.ImmSrc(ImmSrc), .Inst(instruction), .Imm(immediate));
208
209     wire [31:0] jump_adr, NEXT_PC;
210     Adder #(32) (.A(immediate), .B(PCOUT), .S(jump_adr));
211     Adder #(32) (.A(PCOUT), .B(32'd4), .S(NEXT_PC));
212
213     MUX #(3, 32) pc_src_mux (.dataIN({ALU_out, jump_adr, NEXT_PC}), .select(pcsrc), .dataOUT(PCIN));
214     MUX #(4, 32) resultsrc_mux (.dataIN({ALU_out, DataMemOut, NEXT_PC, immediate}), .select(resultsrc), .dataOUT(writeData));
215
216 endmodule
```

Now we need to design the controller. Since we are using single-cycle approach, there is no need for a state machine. All we need is a combinational logic.

Controller

The controller is just a simple lookup table. The rest is just a matter of using “always” blocks and “assign” statements to model the lookup tables. The code was way too long to be included here (170 lines in total). Therefore, we only included snapshots of one of the always blocks, handling “resultsrc” and “regwrite”.

Figure 15. Controller: Result Source Handling Always Block

```
125 always @(opc, f3, f7, ZERO) begin: Result_Source
126     resultsrc_temp = 2'b00;
127     regwrite_temp = 1'b0;
128     if ((opc == ADD_OPC) & (f3 == ADD_F3) & (f7 == ADD_F7)) begin
129         resultsrc_temp = 2'b00; regwrite_temp = 1'b1; end
130     else if ((opc == SUB_OPC) & (f3 == SUB_F3) & (f7 == SUB_F7)) begin
131         resultsrc_temp = 2'b00; regwrite_temp = 1'b1; end
132     else if ((opc == AND_OPC) & (f3 == AND_F3) & (f7 == AND_F7)) begin
133         resultsrc_temp = 2'b00; regwrite_temp = 1'b1; end
134     else if ((opc == OR_OPC) & (f3 == OR_F3) & (f7 == OR_F7)) begin
135         resultsrc_temp = 2'b00; regwrite_temp = 1'b1; end
136     else if ((opc == SLT_OPC) & (f3 == SLT_F3) & (f7 == SLT_F7)) begin
137         resultsrc_temp = 2'b00; regwrite_temp = 1'b1; end
138     else if ((opc == LW_OPC) & (f3 == LW_F3)) begin
139         resultsrc_temp = 2'b01; regwrite_temp = 1'b1; end
140     else if ((opc == ADDI_OPC) & (f3 == ADDI_F3)) begin
141         resultsrc_temp = 2'b00; regwrite_temp = 1'b1; end
142     else if ((opc == XORI_OPC) & (f3 == XORI_F3)) begin
143         resultsrc_temp = 2'b00; regwrite_temp = 1'b1; end
144     else if ((opc == ORI_OPC) & (f3 == ORI_F3)) begin
145         resultsrc_temp = 2'b00; regwrite_temp = 1'b1; end
146     else if ((opc == SLTI_OPC) & (f3 == SLTI_F3)) begin
147         resultsrc_temp = 2'b00; regwrite_temp = 1'b1; end
148     else if ((opc == JALR_OPC) & (f3 == JALR_F3)) begin
149         resultsrc_temp = 2'b10; regwrite_temp = 1'b1; end
150     // else if ((opc == SW_OPC) & (f3 == SW_F3)) begin
151         resultsrc_temp = 2'b; regwrite_temp = 1'b1; end
152     else if ((opc == JAL_OPC)) begin
153         resultsrc_temp = 2'b10; regwrite_temp = 1'b1; end
154     // else if ((opc == BEQ_OPC) & (f3 == BEQ_F3)) begin
155         resultsrc_temp = 2'b; regwrite_temp = 1'b1; end
156     // else if ((opc == BNE_OPC) & (f3 == BNE_F3)) begin
157         resultsrc_temp = 2'b; regwrite_temp = 1'b1; end
158     else if ((opc == LUI_OPC)) begin
159         resultsrc_temp = 2'b11; regwrite_temp = 1'b1; end
160     end
```

Now we can generate the top module and test it.

Top Module

Here's how the top module looks like:

Figure 16. Top Module Verilog Description

```
1  module RISC_V (clk, rst);
2
3      input clk,rst;
4
5      wire regwrite, ALUsrc, memwrite;
6      wire [1:0] pcsrc, resultsrc;
7      wire [2:0] OpCode, ImmSrc;
8      wire clk,rst;
9      wire ZERO;
10     wire [31:0] instruction;
11
12     Datapath DPTH  (pcsrc, ImmSrc, regwrite, ALUsrc, OpCode, memwrite, resultsrc, clk,rst, ZERO, instruction);
13     Controller CNT (instruction, ZERO, pcsrc, ImmSrc, regwrite, ALUsrc, OpCode, memwrite, resultsrc);
14
15 endmodule
```

The only inputs of the top module are clock and reset signals. Since control unit is implemented in a purely combinational manner, it does not need clock or reset signals.

With the top module ready at hand, we could proceed to the testing phase.

Testing Phase

Writing Assembly Code

We were asked to test the processor we implemented with a piece of code that searches an array of 10 integers for its minimum value. Here's how its done in C programming language:

Figure 17. Minimum Finder Code in C language

```
1
2  int i = 0;
3  minimum = A[0];
4  i = i + 1;
5  for(; i < 10 ; i = i + 1){
6      temp = A[i];
7      if(minimum < temp)
8          minimum = temp;
9  }
```

Since we are to implement this in assembly language afterwards, we could change a thing or two to make the conversion easier. Here's the new code, written in a format between assembly and C:

Figure 18. Assembly-Friendly Minimum Finder Code

```
1  int i = 0;
2  minimum = A(i);
3
4  while(1){
5      i = i + 4;
6      if(i >= 40) break;
7      temp = A(i);
8      if(minimum < temp)
9          minimum = temp;
10 }
```

Now this can be easily turned into assembly code. We assumed that the array's first element is located at mem[0x5b0], since that is what we did for this course's second homework to make it compatible with the introduced website. Also, we chose our registers according to the table at the next page.

Register	Purpose	Register Number (X_i)
S_2	Reading data from memory (temp)	X_{18}
S_1	Saving i	X_9
S_0	Saving minimum	X_8
t_1	Saving SLT comparisons' results	X_6

Now we can easily write the assembly code for this.

Figure 19. Assembly Code for Minimum Finder

```

1 | lw s0, 0x5b0(zero)      # minElement = mem[0x5b0] (initialize with the first element)
2 | add s1, zero, zero      # i = 0
3 | Loop:
4 |     addi s1, s1, 4        # i += 4
5 |     slti t1, s1, 40      # check if 10 elements are traversed (40 = 4 * 10)
6 |     beq t1, zero, EndLoop # if 10 elements are traversed, jump to EndLoop
7 |     lw s2, 0x5b0(s1)     # element = mem(i)
8 |     slt t1, s2, s0        # check if element is smaller than minElement
9 |     beq t1, zero, Loop   # if element is not smaller than minElement, jump to Loop
10 |    add s0, s2, zero      # minElement = element
11 |
12 |    jal zero, Loop        # jump to Loop
13 | EndLoop:
14 |    sw s0, 0x5ac(zero)    # mem[2000] = minElement
15 | TRAP:
16 |    jal zero, TRAP

```

All there is left to do is generate machine code from this and fill data and instruction memories.

Generating RISC-V Machine Code

Figure 20. Assembly and Machine Code

1	lw	s0, 0x5b0(zero)	//0x5b002403
2	add	s1, zero, zero	//0x000004b3
3	Loop:		
4	addi	s1, s1, 4	//0x00448493
5	slti	t1, s1, 40	//0x0284a313
6	beq	t1, zero, EndLoop	//0x00030c63
7	lw	s2, 0x5b0(s1)	//0x5b04a903
8	slt	t1, s2, s0	//0x00892333
9	beq	t1, zero, Loop	//0xfe0306e3
10	add	s0, s2, zero	//0x00090433
11			
12	jal	zero, Loop	//0xfe5ff06f
13	EndLoop:		
14	sw	s0, 0x5ac(zero)	//0x5a802623
15	TRAP:		
16	jal	zero TRAP	//0x0000006f

The assembly codes are translated to RISC-V machine language in Hex (the related hex instruction of each line of the assembly code is shown in Figure 21).

To be written in the instruction memory, each hex instruction is first separated into four 2-digit hex numbers, and then written upside down (the 2 least significant hex digits first) in the instruction memory.

for example, the hex instruction 0x5ba40903 is written in the memory like this:

03

09

A4

5b

This reversing is needed for the instructions to be properly read from the memory (2 most significant hex digits first).

We also did this reversing for data to be stored in the data memory. The data we used is this array:

33, 114, 51, 62, -145, -127, 61, 84, 41, 15

Testbench and Results


We used this testbench to test the code:

Figure 22. Top Module Testbench

```
115 module RISC_V_TB();
116
117     reg clk,rst;
118
119     RISC_V UUT (clk, rst);
120
121     initial begin clk = 1 ; rst = 1 ;#25 rst = 1'b0; end
122     always #5 clk = ~clk;
123     initial begin #1000 $stop; end
124
125 endmodule
```

And the memory was updated like this:

Figure 23. Testbench Results

 

This confirms the minimum finding functionality.